

1383

April 2025

Time - Three hours
(Maximum Marks: 100)

[N.B. Answer all the questions, choosing any two subdivision from each question. Each subdivision carries 10 marks.]

1.
 - (a) Describe the operation of half wave rectifier with neat circuit diagram and waveform.
 - (b) Explain the working principle of positive and negative clampers.
 - (c) Explain the working principle of LED with necessary diagrams.
 - (d)
 - (i) What is the function of clipper circuit? Mention its types. (5)
 - (ii) Write a short note on photo diode. (5)
2.
 - (a) Explain the fixed bias transistor circuit with neat sketch.
 - (b)
 - (i) Define biasing. Mention its types. (7)
 - (ii) List out the three modes of BJT. (3)
 - (c) Write the working principle of PNP transistor with a neat sketch.
 - (d) Explain the input and output characteristics of common collector (CC) configuration with neat circuit diagram.
3.
 - (a) Describe the operation of differential amplifier with neat circuit diagram.
 - (b) Write a note on the following:
 - (i) Darlington pair configuration. (7)
 - (ii) CMRR. (3)

[Turn over.....]

- (c) Discuss the operation of transistor as a switch with necessary circuit diagram.
 - (d) Describe the working principle of common emitter amplifier with a neat diagram.
4. (a) (i) Differentiate positive and negative feedback. (5)
(ii) State Barkhausen criterion. (5)
- (b) What is a negative feedback amplifier? Mention its types.
- (c) (i) Draw and explain the tank circuit. (7)
(ii) List the types of oscillator circuits. (3)
- (d) Explain the operation of RC phase shift oscillator with neat sketch.
5. (a) Explain the operation of N channel JFET.
- (b) (i) Compare FET and BJT. (5)
(ii) Draw the equivalent circuit of the UJT. (5)
- (c) Explain the working of N channel depletion mode MOSFET with neat sketch.
- (d) Discuss the operation of UJT with neat sketch.
-